

# Academic Physics: Electricity Review Sheet

## Static Electricity

- Which combinations of charge (positive, negative, neutral) attract?  $+-$   
 $++$   
 $+-$
- Which combinations of charge repel?  $++$   
 $+-$
- What does a lightning rod do? **Attracts + Redirects Lightning**

4. Why are you safe from electricity while inside a hollow metal shell (like a car, house, or plane)?  
**Electricity flows around the outside of Faraday cages!**

- Match each method of charging with how the objects are charged afterwards.
  - Methods**
    - 1. Friction
    - 2. Conduction
    - 3. Polarization
    - 4. Grounding
  - Charges on Objects Afterwards**
    - 1. Both are the same charge
    - 2. + and - are temporarily split up
    - 3. All charge is removed from the object
    - 4. Objects have opposite charge

## Circuit Electricity

$I = V/R$	$V = IR$	$P = IV$	$\text{Energy} = P \cdot t$
$\$ = \text{Energy} \cdot \text{Rate}$			$1 \text{ kW} = 1,000 \text{ W}$
$R_t = R_1 + R_2 + R_3$		$1/R_t = 1/R_1 + 1/R_2 + 1/R_3$	

	Name	Definition	Unit
V	Voltage	Electrical Pressure	Volts
I	Current	Amount of Electricity Flowing	Amps
R	Resistance	Fight against Electric Flow	Ohms, $\Omega$
P	Power	Rate of Electricity Use	Watts, KiloWatts
E	Energy	Unit we get billed in	KWh


- Alternating or Direct? Devices that plug into wall outlets use AC current, while devices that use throwaway batteries use DC current.
- How many volts are in the standard electric outlet in the USA? 120 V AC
- Whether a shock is fatal or not depends primarily on the number of Amps.

- A computer plugs into a 120V outlet, and draws 2 Amps of current. What is the resistance of this computer?  
 $V = I R$   
 $120 = 2 \cdot R$   
 $R = 60 \Omega$
- A toaster has a resistance of 10 ohms and gets plugged into a 120 V outlet.  
A) How much current does it draw?  $I = \frac{V}{R} = \frac{120}{10} = 12 \text{ Amps}$   
 $R = 10 \Omega$   
 $V = 120$

- How much power does the toaster use (in watts and kilowatts)?  
 $P = I V$   
 $(12 \text{ A})(120 \text{ V}) = 1,440 \text{ W} \div 1000 = 1.44 \text{ kW}$
- If you make toast for 6 hours (hungry!) how much does this cost on your electric bill? (Use a rate of \$0.10)  
①  $E = P t$   
 $(1.44 \text{ kW})(6) = 8.64 \text{ kWh}$   
②  $\$ = E \cdot \text{Rate}$   
 $(8.64)(.10) = \$0.864$

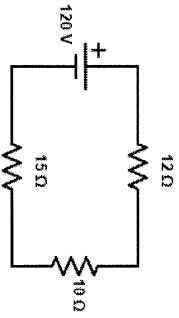
## Series and Parallel Circuits

- What type of circuit is this? **Series**  
a. How many paths for electricity are there? 1  
b. If you unplug a bulb, the others will: Go Out



	Voltage (Volts)	Current (Amps)	Resistance (Ohms)
R1	38.92	3.243	12
R2	32.24	3.243	10
R3	48.64	3.243	15
Total	120	3.243	37

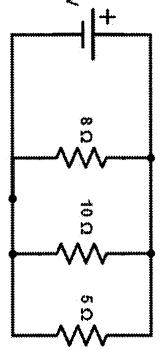- What type of circuit is this? **Parallel**  
a. How many paths for electricity are there? 3  
b. If you unplug a bulb, the others will: Stay On



	Voltage (Volts)	Current (Amps)	Resistance (Ohms)
R1	10	1.25	8
R2	10	1.00	10
R3	10	2.00	5
Total	10	4.25	2.353