

Happy Monday

- On a whiteboard, write the kind of problem that you would like to see solved during the review.

Today

- Study for the quiz.
- Study tonight!

study

(verb)

The act of texting, eating and watching TV with an open textbook nearby.

This Week

- M: Review for quiz
- T: Quiz
- Wednesday: perform your lab
- Thursday: Formal lab report
- Friday: Put together presentation

Electricity Quiz


- Kirchhoff's Rules will be an extra credit problem.
- Static Charges: methods of charging (friction, conduction and induction), attraction and repulsion.
- Circuits: $V=IR$, series circuits, parallel circuits, combined circuits.
- Find the voltage, current and power on each resistor in a circuit.

A PS3 has a power supply of 380W. If the voltage is 120V, what is the resistance of the gaming system?



Three resistors are in a series circuit. The battery is ___ V. The resistors are ___ Ω , ___ Ω and ___ Ω . Find the voltage, current and power at each resistor.

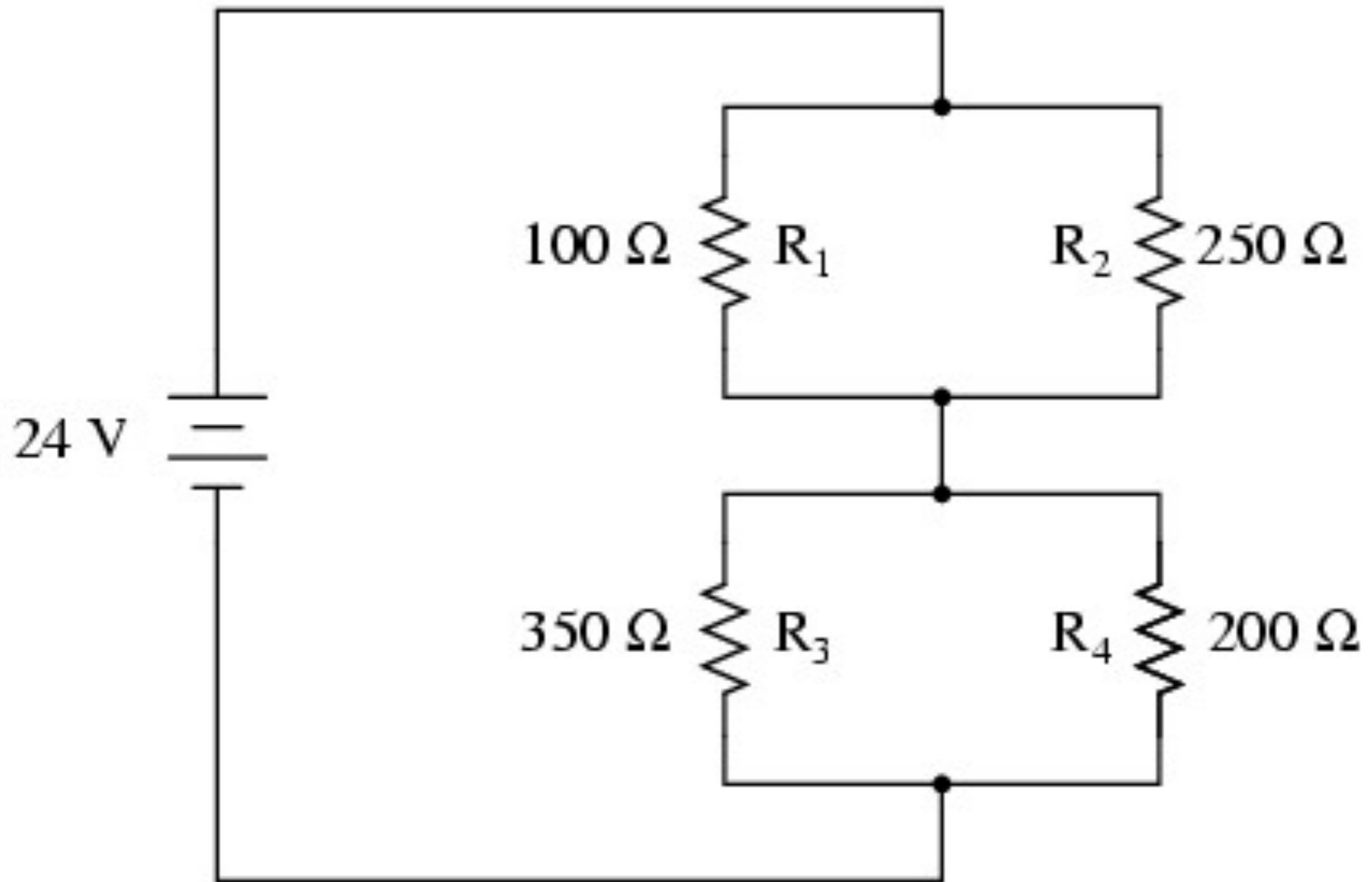
Three resistors are in a parallel circuit. The battery is ___ V. The resistors are ___ Ω , ___ Ω and ___ Ω . Find the voltage, current and power at each resistor.




Determine I , V and P on each resistor

Charging Demo

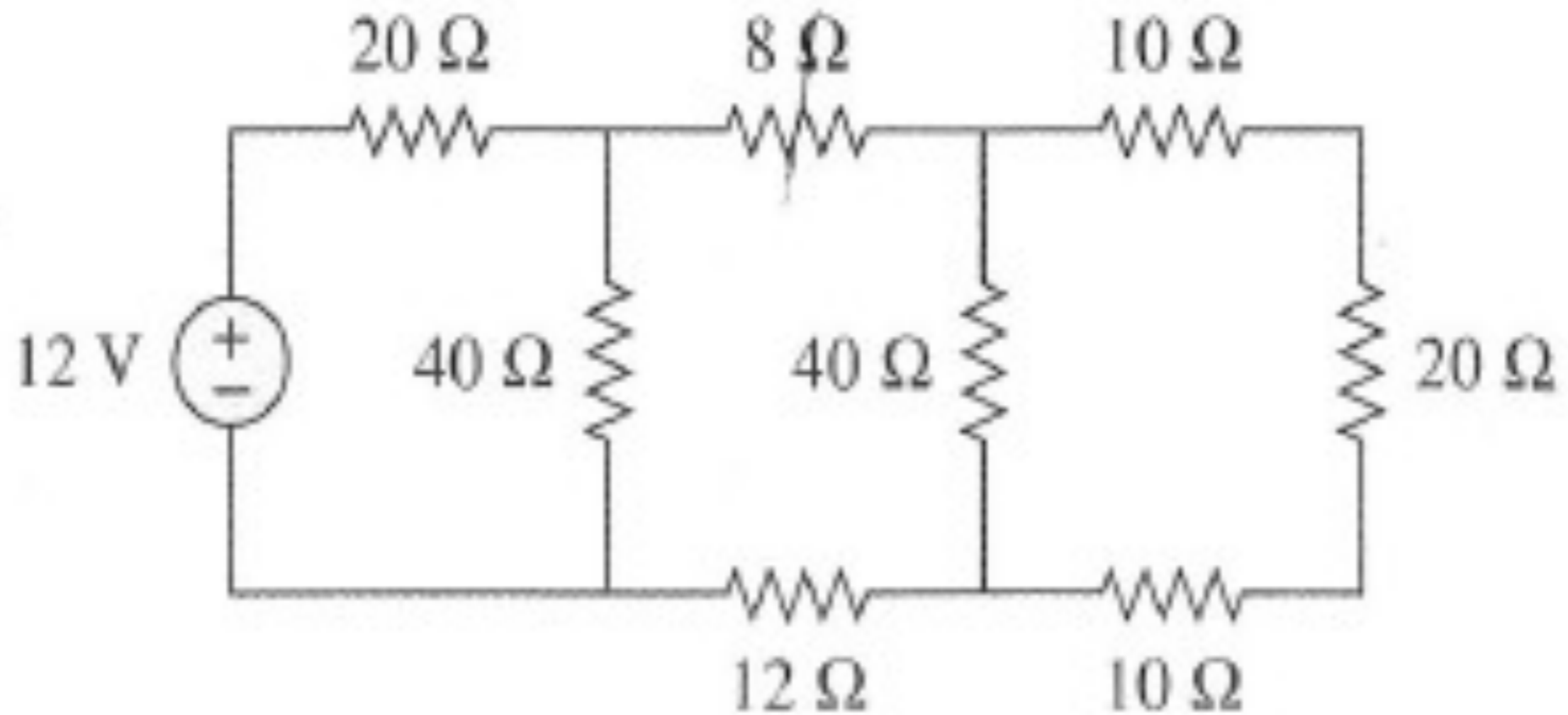- Come to the front of the room and examine the rig that I have set up.
- I will do the demo a few times.
- Name the kinds of charging that occur.
- Options are: friction, induction and conduction.



Determine I , V and P on each resistor

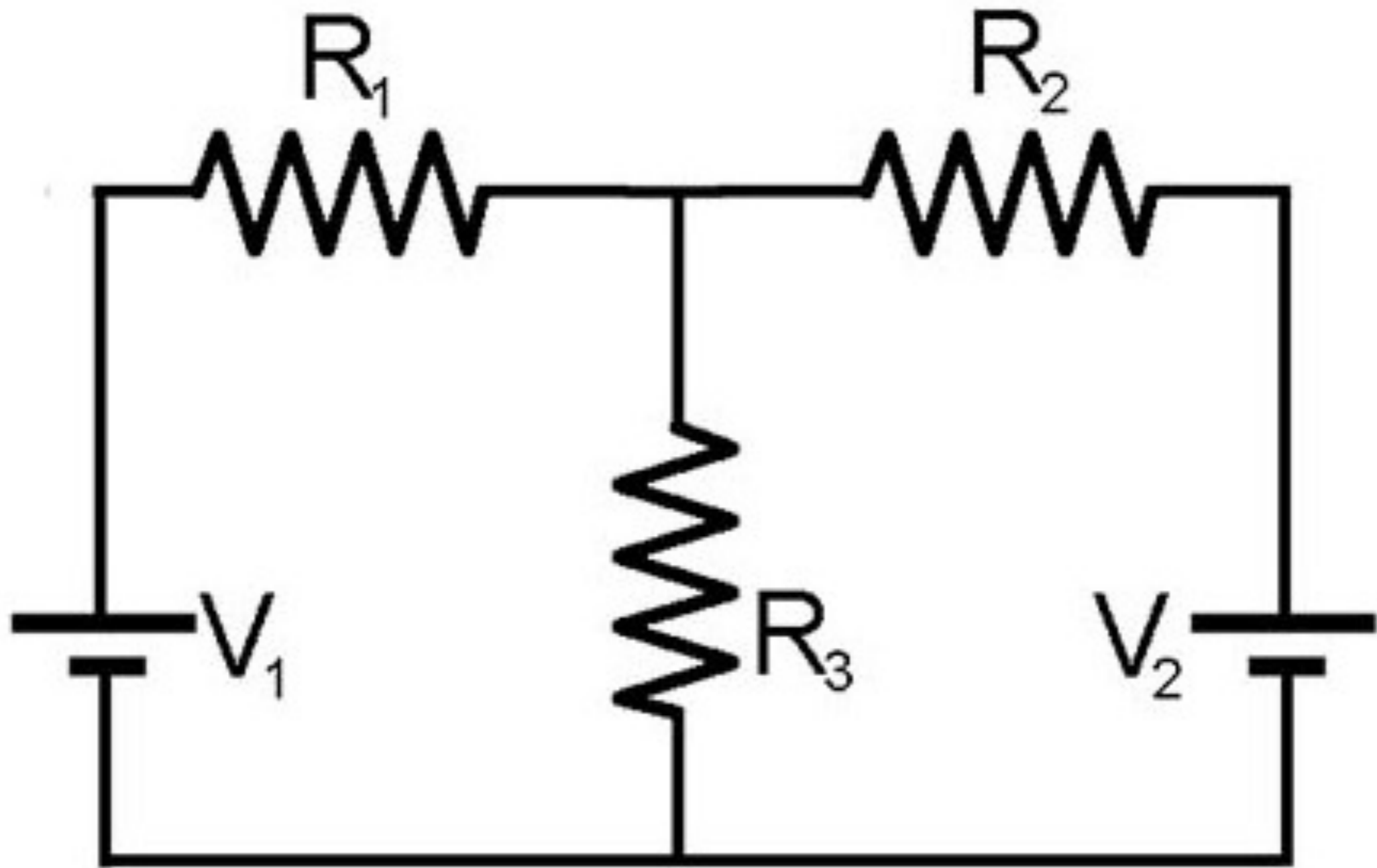

Determine I , V and P on each resistor

Rest of Today

- Read the email that I sent back to you about your lab.
- Make the appropriate changes.
- Finishing touches on lab sheet.