
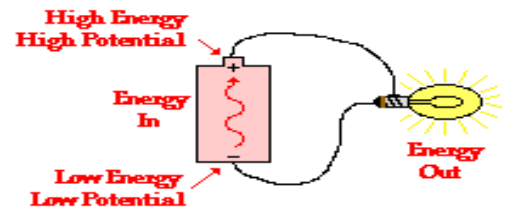


Requirements for an Electric Circuit

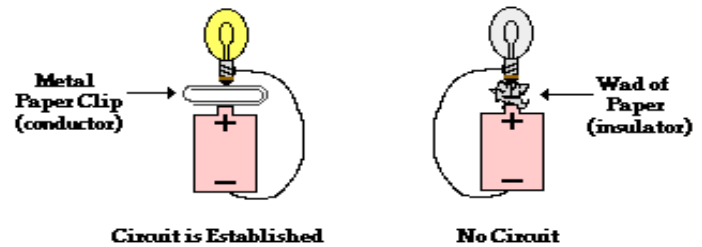1. There must be a _____ conducting path which extends from the _____ terminal to the _____ terminal.
2. All connections must be complete and made by _____ materials capable of _____ charge.
3. There must be an _____ capable of doing _____ on a charge to move it from a _____ location (negative terminal) to a _____ location (positive terminal).
 - *This establishes an electric potential difference across the two ends of the external circuit.*




Circuit Vocabulary

• **Current**

- Current is the _____ of _____
 - *# of charges that pass per second*
- Symbol:
- Units:
- The _____ of an electric current is, by _____, the direction in which a _____ charge would move if placed in the circuit.

• **Voltage**

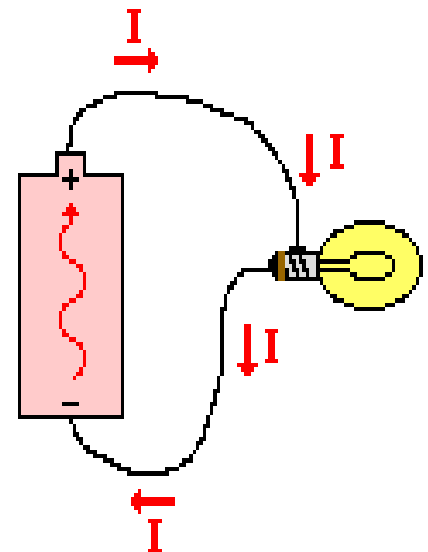- Also defined as electric potential, is the _____ per unit of _____
 - *Energy in a unit of charge*
- Symbol:
- Units:



• **Resistance**

- A _____ to the flow of charge.
- Symbol:
- Units:

Circuit Symbols

- Battery or DC Power Supply
- Wire
- Switch
- Ammeter
- Voltmeter
- Resistor

Ohm's Law

- Current is _____ to Voltage.
 - *If you double voltage, current will _____.*
 - *If you cut voltage in 1/3, current will _____.*
- Current is _____ to Resistance.
 - *If you double resistance, current will _____.*
 - *If you cut voltage in 1/4, current will _____.*
- **Formula:**
- **Examples:**
 - Practice 1: An automobile headlight with a resistance of 30 ohms is placed across a 12-volt battery. What is the current through the circuit?
 - Practice 2: A lamp draws a current of 0.50 amps when it is connected to a 120-V source. What is the resistance of the lamp?
 - Practice 3: A lamp with a resistance of 30 Ω is connected to a voltage source. The current in the circuit is 3.0 A. What is the voltage of the source?

Power

- Measure the _____ at which energy is _____ or _____ from one form of energy to another.
 - *How fast work is being done!*
 - Symbol:
 - Units:
 - **Formula(s):**

Energy

- The amount of _____ being _____ and how _____ it's being used for.
 - Symbol:
 - Units: 1) *if no mention of a time unit:*

2) *if hours mentioned (energy company):*
 - **Formula(s):**

Power & Energy Practice Problems

- A 6.0-V battery delivers a 0.50-A current to an electric motor that is connected across its terminals.
 - What is the power consumed by the motor?

 - If the motor runs for 5.0 minutes, how much electrical energy is delivered?

- A 60 W light bulb is on an average of 7 hours a day.
 - How much energy is used in kilowatt hours (kWh)? $1000\text{ W} = 1\text{ kW}$

 - If it costs \$0.06 per kWh, how much does running this bulb cost per day? Per month (assume 30 days)?

Series Circuits

- There is only _____ for the current to flow.
- Current is the _____ throughout the circuit.
- Resistance _____.
- Voltage _____.

- **Examples:**

- Example 1: Three 20- Ω resistors are connected in series across a 120-V generator.

- a) Draw the circuit
- b) What is the equivalent (total) resistance?
- c) What is the current in the circuit?
- d) What is the potential drop (voltage) across each resistor?

- Example 2: A 3 Ω , 4 Ω and 7 Ω resistor are connected in series across a 12-V battery.

- a) Draw the circuit
- b) What is the equivalent (total) resistance?
- c) What is the current in the circuit?
- d) What is the potential drop (voltage) across each resistor?
- e) What is the power at each resistor?
- f) What is the total power of the circuit?

- Example 3: Four resistors, 45- Ω , 5- Ω , 30- Ω , and 40- Ω are connected in series across a 240-V generator.

- a) What is the equivalent (total) resistance?
- b) What is the current through the entire circuit?
- c) What is the potential drop (voltage) across each resistor?
- d) What is the power at each resistor?
- e) What is the total power of the circuit?

- Example 4: Two resistors, 10- Ω and 30- Ω are connected in series across a 20-V battery.

- a) What is the equivalent (total) resistance?
- b) What is the current through the entire circuit?
- c) What is the potential drop across each resistor?
- d) What is the power drawn by each resistor?
- e) What is the total power of the circuit?

Parallel Circuits

- There are _____ for the current to flow.
- Current _____.
- Equivalent (total) Resistance is always _____ than the smallest resistor.
- Voltage is the _____ throughout the circuit.

- **Examples:**

- Example 1: A 120- Ω resistor, a 60- Ω resistor and a 40- Ω resistor are connected in parallel across a 12-V generator.

- Draw the circuit
- What is the equivalent (total) resistance?
- What is the current through the entire circuit?
- What is the current through each branch of the circuit?

- Example 2: Two resistors, 45- Ω and 5- Ω , are connected in parallel across a 90-V generator.

- Draw the circuit
- What is the equivalent (total) resistance?
- What is the current through the entire circuit?
- What is the current through each branch of the circuit?
- What is the power at each resistor?
- What is the total power of the circuit?

- Example 3: Three resistors, 3- Ω , 12- Ω and 6- Ω , are connected in parallel across a 30-V generator.


- Draw the circuit
- What is the equivalent (total) resistance?
- What is the current through the entire circuit?
- What is the current through each branch of the circuit?
- What is the power at each resistor?
- What is the total power of the circuit?

- Example 4: Two resistors, 24- Ω and 72- Ω , are connected in parallel across a 54-V generator.

- Draw the circuit
- What is the equivalent (total) resistance?
- What is the current through the entire circuit?
- What is the current through each branch of the circuit?
- What is the power at each resistor?
- What is the total power of the circuit?

Combination Circuits – HONORS ONLY

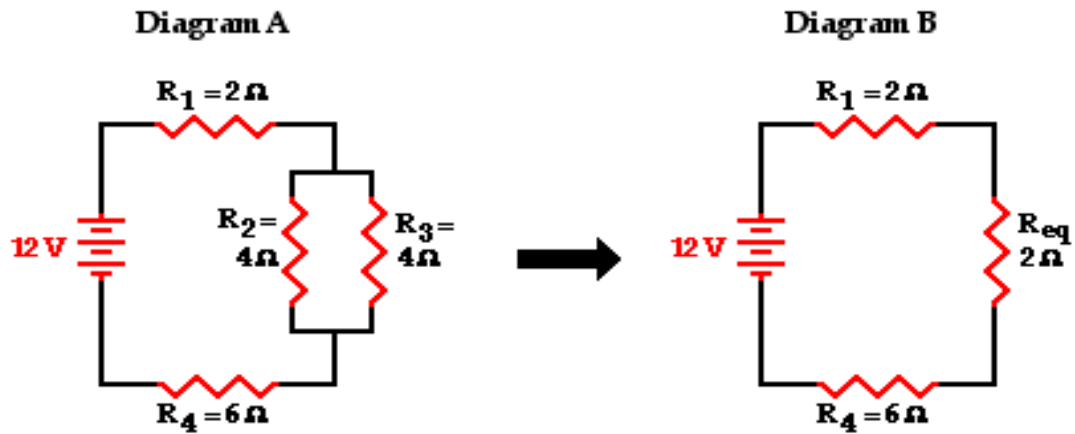- The use of both _____ and _____ connections within the same circuit.
- Use the meaning of _____ for parallel branches to _____ the combination circuit into a _____ circuit.



- **Examples:**

Combination Example 1

$R_{tot} =$ _____	$I_{tot} =$ _____
$I_1 =$ _____	$\Delta V_1 =$ _____
$I_2 =$ _____	$\Delta V_2 =$ _____
$I_3 =$ _____	$\Delta V_3 =$ _____
$I_4 =$ _____	$\Delta V_4 =$ _____

Combination Example 2

$R_{tot} =$ _____	$I_{tot} =$ _____
$I_1 =$ _____	$\Delta V_1 =$ _____
$I_2 =$ _____	$\Delta V_2 =$ _____
$I_3 =$ _____	$\Delta V_3 =$ _____
$I_4 =$ _____	$\Delta V_4 =$ _____