

SERIES $I_{\text{total}} = I_1 = I_2 = I_3$

$$R_{\text{total}} = R_1 + R_2 + R_3$$

$$V_{\text{total}} = V_1 + V_2 + V_3$$

POWER $P = IV = I^2R = \frac{V^2}{R}$

PARALLEL $I_{\text{total}} = I_1 + I_2 + I_3$

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V_{\text{total}} = V_1 = V_2 = V_3$$

ENERGY $E = Pt = IVt = I^2Rt = \frac{V^2t}{R}$

OHMS' LAW $V = IR$

Physics
Unit 4 Review

Name _____
Date _____

1. Suppose you have a 15 A circuit breaker in series with the following parallel combinations all across 120-V: Television – 10 Ω , Alarm Clock – 60 Ω , Lamp – 40 Ω . Can you have all 3 things on at the same time?

2. A curling iron of resistance 80.0 Ω is plugged into a 120-V outlet. How much thermal energy is produced in 2 minutes?

3. A 13.0- Ω resistor and a 52.0- Ω resistor are connected in series and placed across a 130-V generator.
 - a) What is the equivalent resistance of the circuit?

 - b) What is the value of the current in the circuit?

 - c) What is the potential drop (**voltage**) across each resistor?

 - d) Calculate the power of each resistor.

 - e) What is the total power of the circuit?

4. A $3.0\text{-}\Omega$ resistor, a $6.0\text{-}\Omega$ resistor and two $12.0\text{-}\Omega$ resistors are connected in parallel and placed across a 9.0-V power supply.
- What is the equivalent resistance of the circuit?
 - What is the value of the current in each branch of the circuit?
 - What is the value of the total current through the circuit?
 - Calculate the power of each resistor.
 - What is the total power of the circuit?
5. A blow dryer rated at 1500 W is plugged into an outlet of 120-V . What is the resistance of the blow dryer?
6. A digital clock has a resistance of $12,000\ \Omega$ and is plugged into a 115-V outlet.
- How much current does it draw?
 - How much power does it use?
 - If the clock is constantly on (in use 24 hours a day), how much energy in kWh does the clock use in one day?
 - If the owner of the clock pays $\$0.10$ per kWh, how much does it cost to operate the clock for 30 days?
7. Tim left for school at $6:45\text{ a.m.}$ and forgot to turn off his TV, which is rated at 300 W when plugged into a 120-V source. After he came home from school, he left the TV on until leaving for work at $3:45\text{ p.m.}$
- How much energy (in kWh) did the TV use?
 - At $\$0.13$ per kWh, how much did it cost to run the TV?