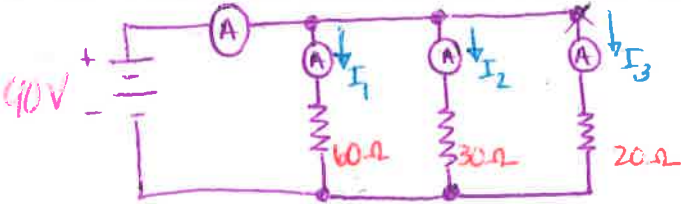


Parallel Circuit Practice Problems

- Remember....
- Equivalent Resistance $\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
 - Current is Added ($I_{\text{total}} = I_1 + I_2 + I_3$)
 - Potential Difference (Voltage) is the Same

1. Three resistors, 60.0-Ω, 30.0-Ω, and 20.0-Ω are connected in parallel across a 90.0-V battery.

a) Draw a diagram and include an ammeter after the battery and before each resistor.



b) Find the current through each branch of the circuit.

$$I_1: 90V = I \cdot 60\Omega \quad I_1 = 1.5A$$

$$I_2: 90V = I \cdot 30\Omega \quad I_2 = 3A$$

$$I_3: 90V = I \cdot 20\Omega \quad I_3 = 4.5A$$

} Total current = 9A

c) Find the equivalent resistance of the circuit.

$$\frac{1}{R_T} = \frac{1}{60} + \frac{1}{30} + \frac{1}{20}$$

$$= \frac{1}{60} + \frac{2}{60} + \frac{3}{60}$$

$$\frac{1}{R_T} = \frac{6}{60} \rightarrow R_T = \frac{60}{6} = 10\Omega$$

Always smaller than smallest resistor

d) Find the current through the battery.

$$V = IR$$

$$90V = I \cdot 10$$

$$I = 9A$$

Power

$$P_1 = 135W$$


$$P_2 = 270W$$

$$P_3 = 405W$$

$$P_T = 810W$$

2. Three 15-Ω resistors are connected in parallel and placed across a 30-V battery.

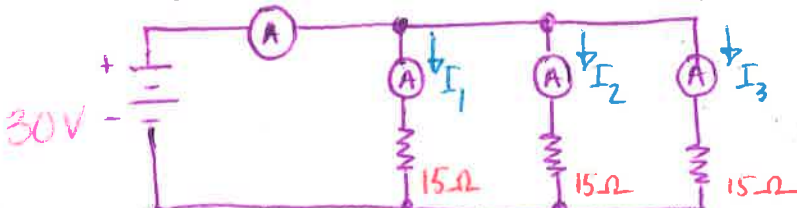a) Draw a diagram and include an ammeter after the battery and before each resistor.



b) What is the equivalent resistance of the parallel circuit?

$$\frac{1}{R_T} = \frac{1}{15} + \frac{1}{15} + \frac{1}{15} = \frac{3}{15} \rightarrow R_T = \frac{15}{3} = 5\Omega$$

Always smaller than smallest resistor

c) What is the current through the entire circuit?

$$V = IR$$

$$30V = I \cdot 5$$

$$I = 6A$$

Power

$$P_1 = 60W$$

$$P_2 = 60W$$

$$P_3 = 60W$$

$$P_T = 180W$$

d) What is the current through each branch of the circuit?

$$I_1 = I_2 = I_3 = 2A$$

$$V = IR$$

$$30 = I \cdot 15 = 2$$

divided by 3 b/c all same resistors